

- *8.29** Derive the state table for the circuit in Figure P8.2. What sequence of input values on wire w is detected by this circuit?

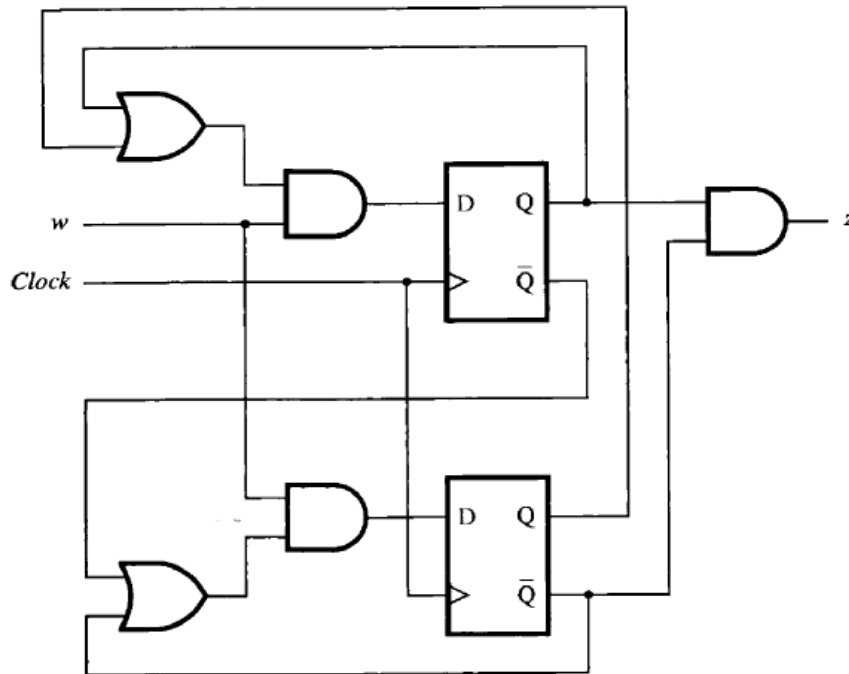


Figure P8.2 Circuit for problem 8.29.

29.

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	C	0
B	A	D	1
C	A	D	0
D	A	B	0

The circuit produces $z = 1$ whenever the input sequence on w comprises a 0 followed by an even number of 1s.

•8.29 Derive the state table for the circuit in Figure P8.2. What sequence of input values on wire w is detected by this circuit?

$$z = s_1 \cdot \bar{s}_2$$

$$y_1 = w(s_1 + s_2)$$

$$y_2 = w(\bar{s}_1 + \bar{s}_2) = w(\overline{s_1 s_2})$$


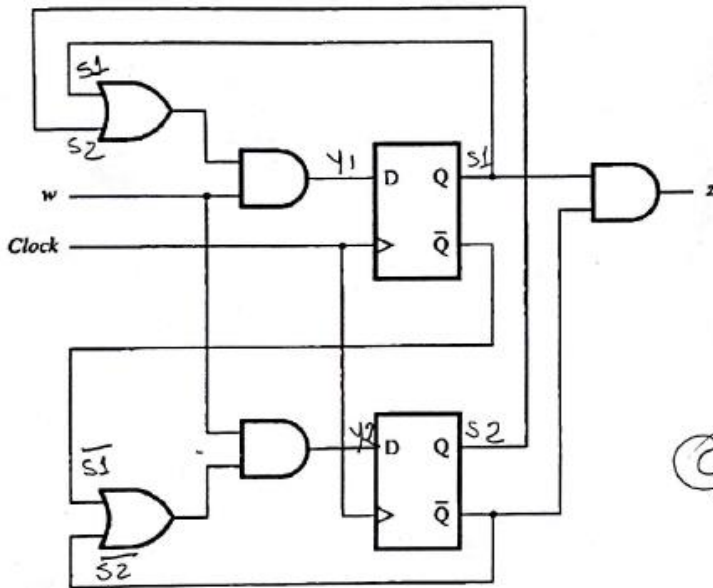


Figure P8.2 Circuit for problem 8.29.

$s_1 s_2$	$w=0$		$w=1$		z
	$y_1 y_2$	$y_1 y_2$	$y_1 y_2$	$y_1 y_2$	
0 0	0 0	0 1	B	0	0
0 1	0 0	1 1	D	0	0
1 0	0 0	1 1	D	1	0
1 1	0 0	1 0	C	0	0

EST. A1	PROX. EST		z
	$w=0$	$w=1$	
A	A	B	0
B	A	D	0
C	A	D	0
D	A	C	0

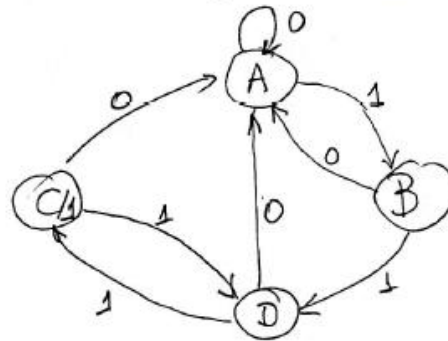

OK

$B \leftrightarrow C$

w	s_1	s_2	y_1	y_2	z
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	1
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	1	0	0

29.

Present state	Next state		Output z
	$w=0$	$w=1$	
A	A	C	0
B	A	D	1
C	A	D	0
D	A	B	0

The circuit produces $z = 1$ whenever the input sequence on w comprises a 0 followed by an even number of 1s.

odd

Present state	Next state $w=0$	Next state $w=1$	Output z
A	A	B	0
B	A	D	1
C	A	D	0
D	A	C	0