

MC542

**Organização de Computadores
Teoria e Prática**

2006

Prof. Paulo Cesar Centoducatte
ducatte@ic.unicamp.br
www.ic.unicamp.br/~ducatte

MC542

Circuitos Lógicos

Circuitos Combinacionais Blocos Básicos


“Fundamentals of Digital Logic with VHDL Design” - (Capítulo 6)

Circuitos Combinacionais: Blocos Básicos

Sumário

- **Multiplexador**
 - Implementação de Funções Lógicas Usando Mux
- **Decodificador**
- **Codificador**
- **Codificador de Prioridade**
- **Conversores**
- **Comparador**
- **VHDL para Circuito Combinacional**
 - Select
 - Atribuição Condicional
 - Processos
 - » If-Then-Else
 - » Case


Multiplexador: 2 para 1 (2:1)

 


Símbolo Gráfico

s	f
0	w ₀
1	w ₁

Tabela Verdade

 


Suma-de-produtos

 


transmission gates


Multiplexador: 4 para 1 (4:1)

 

Mux 4:1 a partir de Mux 2:1


 


Mux 16:1

 




Exemplo de Uso de Mux

2x2 crossbar switch

  


Síntese de Funções Lógicas Usando MUX

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

   

Exemplo

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 


Exemplo

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


$$w_2 \oplus w_3$$

$$\overline{w_2 \oplus w_3}$$

 


Exemplo


w_1	w_2	w_3	f
0	0	0	0
0	0	1	1 } w_3
0	1	0	1 } \bar{w}_3
0	1	1	0 } \bar{w}_3
1	0	0	1 } \bar{w}_3
1	0	1	0 } w_3
1	1	0	0 } w_3
1	1	1	1 }

 


Exemplo Maioria de uns

 

Exemplo Maioria de uns

 


(a) Using a 2-to-1 multiplexer

 



(b) Using a 4-to-1 multiplexer

Decodificador

 


Decodificador 2:4


En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

  


Decodificador 3:8 Usando 2:4

 


Decodificador 4:16 Usando 2:4

 

 Memória $2^m \times n$ read-only memory (ROM)




Codificador

 

2^n -to- n binary encoder

Codificador Binário 4:2

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1


 


Codificador de Prioridade

w_3	w_2	w_1	w_0		y_1	y_0	z
0	0	0	0		d	d	0
0	0	0	1		0	0	1
0	0	1	x		0	1	1
0	1	x	x		1	0	1
1	x	x	x		1	1	1

Exercício: Qual o Circuito Lógico?


Conversor BCD para Código Display de 7 segmentos

  

Display 7-segmentos

w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

Comparador de 4 bits

 

Circuito Combinacional

VHDL

- Comandos de Atribuição:

- Mux 2:1 - Comando Select

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s : IN     STD_LOGIC ;
            f           : OUT    STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    WITH s SELECT
        f <=      w0 WHEN '0',
                    w1 WHEN OTHERS ;
END Behavior ;
```

Circuito Combinacional VHDL

- Mux 4:1 - **Comando Select**

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY mux4to1 IS  
  PORT ( w0, w1, w2, w3 : IN STD_LOGIC ;  
         s             : IN STD_LOGIC_VECTOR(1 DOWNTO 0) ;  
         f             : OUT STD_LOGIC ) ;  
END mux4to1 ;
```

```
ARCHITECTURE Behavior OF mux4to1 IS  
BEGIN  
  WITH s SELECT  
    f <= w0 WHEN "00",  
          w1 WHEN "01",  
          w2 WHEN "10",  
          w3 WHEN OTHERS ;  
END Behavior ;
```

Circuito Combinacional VHDL

- Mux 4:1 - Como um Componente

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
PACKAGE mux4to1_package IS  
COMPONENT mux4to1  
PORT ( w0, w1, w2, w3 : IN STD_LOGIC ;  
       s : IN STD_LOGIC_VECTOR(1 DOWNTO 0) ;  
       f : OUT STD_LOGIC ) ;  
END COMPONENT ;  
END mux4to1_package ;
```

- Mux 16:1 usando o Componente Mux 4:1

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
LIBRARY work ;  
USE work.mux4to1_package.all ;
```

```
ENTITY mux16to1 IS  
    PORT ( w      : IN      STD_LOGIC_VECTOR(0 TO 15) ;  
          s      : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;  
          f      : OUT     STD_LOGIC ) ;  
END mux16to1 ;
```

```
ARCHITECTURE Structure OF mux16to1 IS  
    SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;  
BEGIN  
    Mux1: mux4to1 PORT MAP ( w(0), w(1), w(2), w(3), s(1 DOWNTO 0), m(0) ) ;  
    Mux2: mux4to1 PORT MAP ( w(4), w(5), w(6), w(7), s(1 DOWNTO 0), m(1) ) ;  
    Mux3: mux4to1 PORT MAP ( w(8), w(9), w(10), w(11), s(1 DOWNTO 0), m(2) ) ;  
    Mux4: mux4to1 PORT MAP ( w(12), w(13), w(14), w(15), s(1 DOWNTO 0), m(3) ) ;  
    Mux5: mux4to1 PORT MAP  
        ( m(0), m(1), m(2), m(3), s(3 DOWNTO 2), f ) ;  
END Structure ;
```

Decodificador Binário

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           En     : IN      STD_LOGIC ;
           y      : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;

ARCHITECTURE Behavior OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "1000" WHEN "100",
                    "0100" WHEN "101",
                    "0010" WHEN "110",
                    "0001" WHEN "111",
                    "0000" WHEN OTHERS ;
END Behavior ;
```

Circuito Combinacional

VHDL

- Mux 2:1 Comando *Condicional*

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s      : IN      STD_LOGIC ;
           f            : OUT      STD_LOGIC ) ;
END mux2to1 ;
```

```
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    f <= w0 WHEN s = '0' ELSE w1 ;
END Behavior ;
```

Circuito Combinacional

VHDL

- Processo (mux 2:1)
 - Comando IF-Then-Else

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s      : IN      STD_LOGIC ;
           f            : OUT      STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        IF s = '0' THEN
            f <= w0 ;
        ELSE
            f <= w1 ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Circuito Combinacional

VHDL

- Processo (mux 2:1 - alternativo)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s      : IN      STD_LOGIC ;
            f           : OUT     STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        f <= w0 ;
        IF s = '1' THEN
            f <= w1 ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Exercício: Qual o Bloco implementado?

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY priority IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
           y      : OUT     STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           z      : OUT      STD_LOGIC ) ;
END priority ;
```

ARCHITECTURE Behavior OF xxxxxxx? IS

```
BEGIN
PROCESS ( w )
BEGIN
    IF w(3) = '1' THEN
        y <= "11" ;
    ELSIF w(2) = '1' THEN
        y <= "10" ;
    ELSIF w(1) = '1' THEN
        y <= "01" ;
    ELSE
        y <= "00" ;
    END IF ;
END PROCESS ;
z <= '0' WHEN w = "0000" ELSE '1' ;
END Behavior ;
```

- Processo (Comando **Case**)

Circuito Combinacional VHDL

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY mux2to1 IS  
    PORT ( w0, w1, s : IN STD_LOGIC ;  
           f          : OUT STD_LOGIC ) ;  
END mux2to1 ;  
  
ARCHITECTURE Behavior OF mux2to1 IS  
BEGIN  
    PROCESS ( w0, w1, s )  
    BEGIN  
        CASE s IS  
            WHEN '0' =>  
                f <= w0 ;  
            WHEN OTHERS =>  
                f <= w1 ;  
        END CASE ;  
    END PROCESS ;  
END Behavior ;
```

Decodificador de 7 segmentos

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY seg7 IS
    PORT ( bcd : IN STD_LOGIC_VECTOR(3 DOWNTO 0) ;
            leds : OUT STD_LOGIC_VECTOR(1 TO 7) ) ;
END seg7 ;
ARCHITECTURE Behavior OF seg7 IS
BEGIN
    PROCESS ( bcd )
    BEGIN
        CASE bcd IS
            WHEN "0000" => leds <= "1111110" ;
            WHEN "0001" => leds <= "0110000" ;
            WHEN "0010" => leds <= "1101101" ;
            WHEN "0011" => leds <= "1111001" ;
            WHEN "0100" => leds <= "0110011" ;
            WHEN "0101" => leds <= "1011011" ;
            WHEN "0110" => leds <= "1011111" ;
            WHEN "0111" => leds <= "1110000" ;
            WHEN "1000" => leds <= "1111111" ;
            WHEN "1001" => leds <= "1110011" ;
            WHEN OTHERS => leds <= "-----" ;
        END CASE ;
    END PROCESS ;
END Behavior ;
```

74381 ALU

Operation	Inputs	Outputs
	$s_2 \ s_1 \ s_0$	F
Clear	0 0 0	0 0 0 0
B-A	0 0 1	$B - A$
A-B	0 1 0	$A - B$
ADD	0 1 1	$A + B$
XOR	1 0 0	$A \text{ XOR } B$
OR	1 0 1	$A \text{ OR } B$
AND	1 1 0	$A \text{ AND } B$
Preset	1 1 1	1 1 1 1

74381 ALU

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE ieee.std_logic_unsigned.all ;
```

```
ENTITY alu IS  
    PORT ( s      : IN      STD_LOGIC_VECTOR(2 DOWNTO 0) ;  
          A, B   : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;  
          F      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;  
END alu ;
```

74381 ALU

ARCHITECTURE Behavior OF alu IS

BEGIN

PROCESS (s, A, B)

BEGIN

CASE s IS

WHEN "000" =>

F <= "0000" ;

WHEN "001" =>

F <= B - A ;

WHEN "010" =>

F <= A - B ;

WHEN "011" =>

F <= A + B ;

WHEN "100" =>

F <= A XOR B ;

WHEN "101" =>

F <= A OR B ;

WHEN "110" =>

F <= A AND B ;

WHEN OTHERS =>

F <= "1111" ;

END CASE ;

END PROCESS ;

END Behavior ;

74381 ALU

