

MC542

Organização de Computadores Teoria e Prática

2006

Prof. Paulo Cesar Centoducatte

ducatte@ic.unicamp.br

www.ic.unicamp.br/~ducatte

MC542

Circuitos Lógicos

**Projeto de Flip-Flops, Registradores,
Contadores com VHDL**

**“Fundamentals of Digital Logic with VHDL
Design” - (Capítulo 7)**

Título do Capítulo Abordado

Sumário


- **Memória Implícita**
- **FF D da Biblioteca**
- **Gated D latch**
- **Flip-Flop D**
 - Usando Wait Until
 - Com reset Assíncrono
- **Módulo lpm_shiftreg**
- **Registrador**
 - 8 bits com Clear Assíncrono
 - N bits com Clear Assíncrono
- **Flip-flop D com um mux 2:1 na entrada D**

Memória Implícita

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY implied IS  
    PORT ( A, B      : IN      STD_LOGIC ;  
           AeqB      : OUT    STD_LOGIC ) ;  
END implied ;  
  
ARCHITECTURE Behavior OF implied IS  
BEGIN  
    PROCESS ( A, B )  
    BEGIN  
        IF A = B THEN  
            AeqB <= '1' ;  
        END IF ;  
    END PROCESS ;  
END Behavior ;
```

Memória Implícita
 
```
...  
PROCESS ( A, B )  
BEGIN  
    IF A = B THEN  
        AeqB <= '1' ;  
    END IF ;  
END PROCESS ;  
...
```



Instanciação de um FF D da Biblioteca

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
LIBRARY altera ;  
USE altera.maxplus2.all ;
```

```
ENTITY flipflop IS
```

```
    PORT ( D, Clock           : IN     STD_LOGIC ;  
          Resetn, Presetn     : IN     STD_LOGIC ;  
          Q                   : OUT    STD_LOGIC ) ;
```

```
END flipflop ;
```

```
ARCHITECTURE Structure OF flipflop IS
```

```
BEGIN
```

```
    dff_instance: dff PORT MAP ( D, Clock, Resetn, Presetn, Q ) ;
```

```
END Structure ;
```

Gated D latch

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY latch IS
    PORT ( D, Clk : IN     STD_LOGIC ;
          Q      : OUT    STD_LOGIC) ;
END latch ;

ARCHITECTURE Behavior OF latch IS
BEGIN
    PROCESS ( D, Clk )
    BEGIN
        IF Clk = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Flip-Flop D

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY flipflop IS  
    PORT (    D, Clock  : IN  STD_LOGIC ;  
            Q          : OUT STD_LOGIC) ;  
END flipflop ;  
  
ARCHITECTURE Behavior OF flipflop IS  
BEGIN  
    PROCESS ( Clock )  
    BEGIN  
        IF Clock'EVENT AND Clock = '1' THEN  
            Q <= D ;  
        END IF ;  
    END PROCESS ;  
END Behavior ;
```


Flip-Flop D Usando Wait Until

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY flipflop IS  
    PORT ( D, Clock : IN      STD_LOGIC ;  
           Q          : OUT    STD_LOGIC ) ;  
END flipflop ;  
  
ARCHITECTURE Behavior OF flipflop IS  
BEGIN  
    PROCESS  
    BEGIN  
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;  
        Q <= D ;  
    END PROCESS ;  
END Behavior ;
```

Flip-Flop D com reset Assíncrono

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN    STD_LOGIC ;
          Q                 : OUT   STD_LOGIC) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Flip-Flop D com Reset Síncrono

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY flipflop IS  
    PORT ( D, Resetn, Clock : IN    STD_LOGIC ;  
           Q                 : OUT  STD_LOGIC) ;  
END flipflop ;  
  
ARCHITECTURE Behavior OF flipflop IS  
BEGIN  
    PROCESS  
    BEGIN  
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;  
        IF Resetn = '0' THEN  
            Q <= '0' ;  
        ELSE  
            Q <= D ;  
        END IF ;  
    END PROCESS ;  
END Behavior ;
```

Módulo lpm_shiftreg

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
LIBRARY lpm ;  
USE lpm.lpm_components.all ;
```

```
ENTITY shift IS
```

```
    PORT ( Clock      : IN      STD_LOGIC ;  
          Reset       : IN      STD_LOGIC ;  
          Shiftin, Load : IN      STD_LOGIC ;  
          R           : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;  
          Q           : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
```

```
END shift ;
```

```
ARCHITECTURE Structure OF shift IS
```

```
BEGIN
```

```
    instance: lpm_shiftreg
```

```
        GENERIC MAP (LPM_WIDTH => 4, LPM_DIRECTION => "RIGHT")
```

```
        PORT MAP (data => R, clock => Clock, aclr => Reset,  
                 load => Load, shiftin => Shiftin, q => Q ) ;
```

```
END Structure ;
```

Registrador de 8 bits com Clear Assíncrono

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY reg8 IS
    PORT ( D           : IN   STD_LOGIC_VECTOR(7 DOWNTO 0) ;
          Resetn, Clock : IN   STD_LOGIC ;
          Q           : OUT  STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;
END reg8 ;

ARCHITECTURE Behavior OF reg8 IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= "00000000" ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Registrador de N bits com Clear Assíncrono

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY regn IS
    GENERIC ( N : INTEGER := 16 ) ;
    PORT (D           : IN  STD_LOGIC_VECTOR(N-1 DOWNT0 0);
          Resetn, Clock : IN  STD_LOGIC ;
          Q           : OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0) );
END regn ;

ARCHITECTURE Behavior OF regn IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= (OTHERS => '0') ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Flip-flop D com um mux 2:1 na entrada D

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY muxdff IS
    PORT ( D0, D1, Sel, Clock : IN          STD_LOGIC ;
          Q           : OUT STD_LOGIC ) ;
END muxdff ;

ARCHITECTURE Behavior OF muxdff IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF Sel = '0' THEN
            Q <= D0 ;
        ELSE
            Q <= D1 ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Shift Register

Usando muxdff como Componente

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY shift4 IS
    PORT ( R          : IN          STD_LOGIC_VECTOR(3 DOWNTO 0);
          L, w, Clock : IN          STD_LOGIC ;
          Q          : BUFFER      STD_LOGIC_VECTOR(3 DOWNTO 0));
END shift4 ;

ARCHITECTURE Structure OF shift4 IS
    COMPONENT muxdff
        PORT ( D0, D1, Sel, Clock : IN          STD_LOGIC ;
              Q          : OUT STD_LOGIC ) ;
    END COMPONENT ;
BEGIN
    Stage3: muxdff PORT MAP ( w, R(3), L, Clock, Q(3) ) ;
    Stage2: muxdff PORT MAP ( Q(3), R(2), L, Clock, Q(2) ) ;
    Stage1: muxdff PORT MAP ( Q(2), R(1), L, Clock, Q(1) ) ;
    Stage0: muxdff PORT MAP ( Q(1), R(0), L, Clock, Q(0) ) ;
END Structure ;
```


Shift Register Código Alternativo

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY shift4 IS
    PORT ( R      : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Clock  : IN      STD_LOGIC ;
          L, w   : IN      STD_LOGIC ;
          Q      : BUFFER  STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END shift4 ;
```

```
ARCHITECTURE Behavior OF shift4 IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF L = '1' THEN
            Q <= R ;
        ELSE
            Q(0) <= Q(1) ;
            Q(1) <= Q(2);
            Q(2) <= Q(3) ;
            Q(3) <= w ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Shift Register de N bits

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY shiftn IS
    GENERIC ( N : INTEGER := 8 ) ;
    PORT ( R      : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
          Clock  : IN      STD_LOGIC ;
          L, w    : IN      STD_LOGIC ;
          Q      : BUFFER  STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END shiftn ;
ARCHITECTURE Behavior OF shiftn IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF L = '1' THEN
            Q <= R ;
        ELSE
            Genbits: FOR i IN 0 TO N-2 LOOP
                Q(i) <= Q(i+1) ;
            END LOOP ;
            Q(N-1) <= w ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Contador de 4 Bits (Crescente)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY upcount IS
    PORT ( Clock, Resetn, E : IN  STD_LOGIC ;
          Q           : OUT  STD_LOGIC_VECTOR (3 DOWNTO 0)) ;
END upcount ;
```

```
ARCHITECTURE Behavior OF upcount IS
    SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNTO 0) ;
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Count <= "0000" ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF E = '1' THEN
                Count <= Count + 1 ;
            ELSE
                Count <= Count ;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Count ;
END Behavior ;
```

Contador Usando Sinal Tipo Integer

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY upcount IS
    PORT ( R          : IN      INTEGER RANGE 0 TO 15 ;
          Clock, Resetn, L : IN      STD_LOGIC ;
          Q          : BUFFER  INTEGER RANGE 0 TO 15 ) ;
END upcount ;

ARCHITECTURE Behavior OF upcount IS
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Q <= 0 ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF L = '1' THEN
                Q <= R ;
            ELSE
                Q <= Q + 1 ;
            END IF;
        END IF;
    END PROCESS;
END Behavior;
```

Contador Decrescente

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY downcnt IS
    GENERIC ( modulus : INTEGER := 8 ) ;
    PORT ( Clock, L, E : IN STD_LOGIC ;
          Q           : OUT  INTEGER RANGE 0 TO modulus-1 ) ;
END downcnt ;
```

```
ARCHITECTURE Behavior OF downcnt IS
    SIGNAL Count : INTEGER RANGE 0 TO modulus-1 ;
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL (Clock'EVENT AND Clock = '1') ;
        IF E = '1' THEN
            IF L = '1' THEN
                Count <= modulus-1 ;
            ELSE
                Count <= Count-1 ;
            END IF ;
        END IF ;
    END PROCESS;
    Q <= Count ;
END Behavior ;
```

Registrador de N bits

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY regn IS
    GENERIC ( N : INTEGER := 8 ) ;
    PORT ( R          : IN   STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
          Rin, Clock  : IN   STD_LOGIC ;
          Q           : OUT  STD_LOGIC_VECTOR(N-1 DOWNTO 0) ) ;
END regn ;

ARCHITECTURE Behavior OF regn IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF Rin = '1' THEN
            Q <= R ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Registrador N bits com Saída Tri-state

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY trin IS
    GENERIC ( N : INTEGER := 8 ) ;
    PORT ( X   : IN   STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
          E   : IN   STD_LOGIC ;
          F   : OUT  STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END trin ;

ARCHITECTURE Behavior OF trin IS
BEGIN
    F <= (OTHERS => 'Z') WHEN E = '0' ELSE X ;
END Behavior ;
```

Decclaração de Um Package

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
PACKAGE components IS
```

```
    COMPONENT regn -- register
```

```
        GENERIC ( N : INTEGER := 8 ) ;
```

```
        PORT (   R           : IN     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;  
                Rin, Clock  : IN     STD_LOGIC ;  
                Q           : OUT    STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
```

```
    END COMPONENT ;
```

```
    COMPONENT shiftr -- left-to-right shift register with async reset
```

```
        GENERIC ( K : INTEGER := 4 ) ;
```

```
        PORT (   Resetn, Clock, w : IN     STD_LOGIC ;  
                Q                 : BUFFER STD_LOGIC_VECTOR(1 TO K) ) ;
```

```
    END component ;
```

```
    COMPONENT trin -- tri-state buffers
```

```
        GENERIC ( N : INTEGER := 8 ) ;
```

```
        PORT (   X : IN  STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;  
                E : IN  STD_LOGIC ;  
                F : OUT  STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
```

```
    END COMPONENT ;
```

```
END components ;
```