

# MC542

## Organização de Computadores Teoria e Prática

2006

Prof. Paulo Cesar Centoducatte

[ducatte@ic.unicamp.br](mailto:ducatte@ic.unicamp.br)

[www.ic.unicamp.br/~ducatte](http://www.ic.unicamp.br/~ducatte)

**MC542**

## **Circuitos Lógicos**

**Projeto de Máquinas de Estados  
com VHDL**

**“Fundamentals of Digital Logic with VHDL  
Design” - (Capítulo 8)**

# Projeto de Máquinas de Estados com VHDL

## Sumário

- Código VHDL para FSM de Moore
- Código VHDL para FSM de Mealy

# FSM de Moore

```
USE ieee.std_logic_1164.all ;
```

```
ENTITY simple IS
```

```
    PORT (Clock, Resetn, w : IN    STD_LOGIC ;  
          z                : OUT  STD_LOGIC ) ;
```

```
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    TYPE State_type IS (A, B, C) ; -- Tipo Enumerado para  
                                   -- definir os Estados
```

```
    SIGNAL y : State_type ;
```

```
BEGIN
```

```
    PROCESS ( Resetn, Clock )
```

```
    BEGIN
```

```
        IF Resetn = '0' THEN
```


```
            y <= A ;
```

```
        ELSIF (Clock'EVENT AND Clock = '1') THEN
```


```
con't ...
```
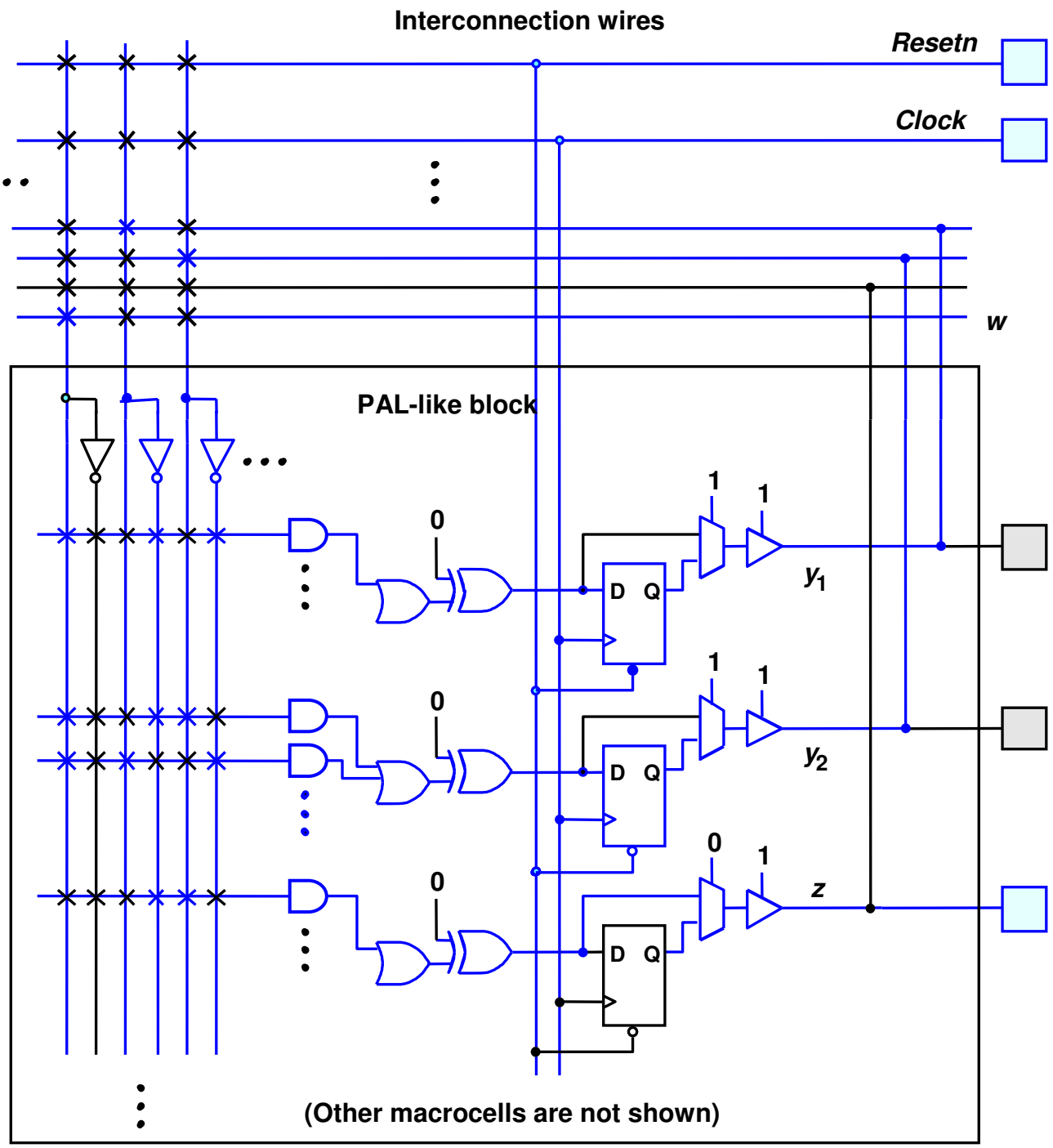
# FSM de Moore


```
CASE y IS
  WHEN A =>
    IF w = '0'
      THEN y <= A ;
      ELSE y <= B ;
    END IF ;
  WHEN B =>
    IF w = '0'
      THEN y <= A ;
      ELSE y <= C ;
    END IF ;
  WHEN C =>
    IF w = '0'
      THEN y <= A ;
      ELSE y <= C ;
    END IF ;
END CASE ;
END IF ;
END PROCESS ;
z <= '1' WHEN y = C ELSE '0' ;
END Behavior ;
```



# FSM de Moore Simulação

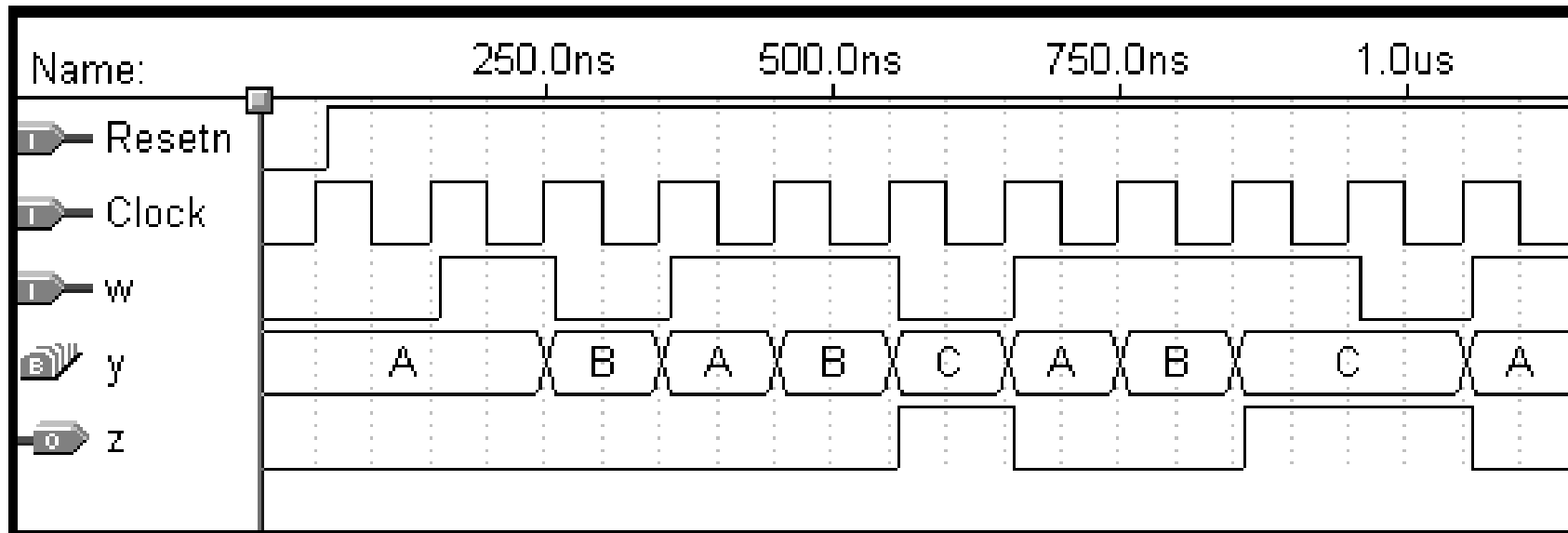

# FSM de Moore Simulação

 



## FSM de Moore Codificação Alternativa

```
USE ieee.std_logic_1164.all ;
```

```
ENTITY simple IS
```

```
    PORT (Clock, Resetn, w : IN    STD_LOGIC ;  
          z                : OUT  STD_LOGIC ) ;
```

```
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    TYPE State_type IS (A, B, C) ;
```

```
    SIGNAL y_present, y_next : State_type ;
```

# FSM de Moore

## Codificação Alternativa

```
BEGIN
  PROCESS ( w, y_present )
  BEGIN
    CASE y_present IS
      WHEN A =>
        IF w = '0' THEN
          y_next <= A ;
        ELSE
          y_next <= B ;
        END IF ;
      WHEN B =>
        IF w = '0' THEN
          y_next <= A ;
        ELSE
          y_next <= C ;
        END IF ;
```

# FSM de Moore

## Codificação Alternativa

```
        WHEN C =>
            IF w = '0' THEN
                y_next <= A ;
            ELSE
                y_next <= C ;
            END IF ;
        END CASE ;
    END PROCESS ;

    PROCESS (Clock, Resetn)
    BEGIN
        IF Resetn = '0' THEN
            y_present <= A ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            y_present <= y_next ;
        END IF ;
    END PROCESS ;

    z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;
```

# FSM

## O Usuário Especificando a Atribuição de Estados

```
ARCHITECTURE Behavior OF simple IS
```

```
TYPE State_TYPE IS (A, B, C) ;
```

```
ATTRIBUTE ENUM_ENCODING : STRING ;
```

```
ATTRIBUTE ENUM_ENCODING OF State_type : TYPE IS "00 01 11";
```

```
SIGNAL y_present, y_next : State_type ;
```

```
BEGIN
```

```
con't ...
```

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY simple IS  
    PORT ( Clock, Resetn, w : IN      STD_LOGIC ;  
          z                               : OUT  
          STD_LOGIC ) ;  
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    SIGNAL y_present, y_next : STD_LOGIC_VECTOR(1 DOWNTO 0);  
    CONSTANT A  : STD_LOGIC_VECTOR(1 DOWNTO 0) := "00" ;  
    CONSTANT B  : STD_LOGIC_VECTOR(1 DOWNTO 0) := "01" ;  
    CONSTANT C  : STD_LOGIC_VECTOR(1 DOWNTO 0) := "11" ;  
  
BEGIN  
    PROCESS ( w, y_present )  
    BEGIN  
        CASE y_present IS  
            WHEN A =>  
                IF w = '0' THEN y_next <= A ;  
                ELSE y_next <= B ;  
                END IF ;
```

... con't

```

        WHEN B =>
            IF w = '0' THEN y_next <= A ;
            ELSE y_next <= C ;
            END IF ;
        WHEN C =>
            IF w = '0' THEN y_next <= A ;
            ELSE y_next <= C ;
            END IF ;
        WHEN OTHERS =>
            y_next <= A ;
    END CASE ;
END PROCESS ;

```

```

PROCESS ( Clock, Resetn )
BEGIN
    IF Resetn = '0' THEN
        y_present <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;
z <= '1' WHEN y_present = C ELSE '0' ;

```

END Behavior ;

# FSM de Mealy

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mealy IS
    PORT ( Clock, Resetn, w      : IN  STD_LOGIC ;
          z                      : OUT STD_LOGIC ) ;
END mealy ;

ARCHITECTURE Behavior OF mealy IS
    TYPE State_type IS (A, B) ;
    SIGNAL y : State_type ;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            y <= A ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            CASE y IS
                WHEN A =>
                    IF w = '0' THEN y <= A ;
                    ELSE y <= B ;
                    END IF ;
            END CASE ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

... con't

# FSM de Mealy

```
                WHEN B =>
                    IF w = '0' THEN y <= A ;
                    ELSE y <= B ;
                    END IF ;
            END CASE ;
    END IF ;
END PROCESS ;

PROCESS ( y, w )
BEGIN
    CASE y IS
        WHEN A =>
            z <= '0' ;
        WHEN B =>
            z <= w ;
    END CASE ;
END PROCESS ;
END Behavior ;
```



# FSM de Mealy

- Estudar 8.5 a 8.8 (exemplos de projetos)