

MC542

Organização de Computadores Teoria e Prática

2007

Prof. Paulo Cesar Centoducatte

ducatte@ic.unicamp.br

www.ic.unicamp.br/~ducatte

MC542

Circuitos Lógicos

VHDL

Flip-Flops, Registradores, Máquinas de Estados

Título do Capítulo Abordado

Sumário

- Instanciação de um FF D da Biblioteca
- Gated D latch
- Flip-Flop D
- Flip-Flop D Usando Wait Until
- Flip-Flop D com Reset Assíncrono
- Flip-Flop D com Reset Síncrono
- Módulo lpm_shiftreg
- Registrador de 8 bits com Clear Assíncrono
- Registrador de N bits com Clear Assíncrono
- Flip-flop D com um mux 2:1 na entrada D
- Shift Register Usando muxdff como Componente
- Shift Register Código Alternativo
- Registrador N bits com Saída Tri-state
- Código VHDL para FSM de Moore
- Código VHDL para FSM de Mealy

Instanciação de um FF D da Biblioteca

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
LIBRARY altera;  
USE altera.maxplus2.all;
```

```
ENTITY flipflop IS  
    PORT ( D, Clock      : IN    STD_LOGIC;  
          Resetn, Presetn : IN    STD_LOGIC;  
          Q               : OUT   STD_LOGIC );  
END flipflop;
```

```
ARCHITECTURE Structure OF flipflop IS  
BEGIN  
    dff_instance: dff PORT MAP ( D, Clock, Resetn, Presetn, Q );  
END Structure;
```

Gated D latch

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY latch IS
    PORT ( D, Clk : IN    STD_LOGIC;
          Q       : OUT  STD_LOGIC);
END latch;

ARCHITECTURE Behavior OF latch IS
BEGIN
    PROCESS ( D, Clk )
    BEGIN
        IF Clk = '1' THEN
            Q <= D;
        END IF;
    END PROCESS;
END Behavior;
```

Flip-Flop D

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY flipflop IS  
    PORT ( D, Clock    : IN    STD_LOGIC;  
          Q             : OUT  STD_LOGIC);  
END flipflop;  
  
ARCHITECTURE Behavior OF flipflop IS  
BEGIN  
    PROCESS ( Clock )  
    BEGIN  
        IF Clock'EVENT AND Clock = '1' THEN  
            Q <= D;  
        END IF;  
    END PROCESS;  
END Behavior;
```

Flip-Flop D Usando Wait Until

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY flipflop IS
    PORT (D, Clock : IN  STD_LOGIC;
          Q       : OUT STD_LOGIC );
END flipflop;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1';
        Q <= D;
    END PROCESS;
END Behavior;
```

Flip-Flop D com Reset Assíncrono

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY flipflop IS
```

```
    PORT ( D, Resetn, Clock : IN    STD_LOGIC;
```

```
          Q                  : OUT STD_LOGIC);
```

```
END flipflop;
```

```
ARCHITECTURE Behavior OF flipflop IS
```

```
BEGIN
```

```
    PROCESS ( Resetn, Clock )
```

```
    BEGIN
```

```
        IF Resetn = '0' THEN
```

```
            Q <= '0';
```

```
        ELSIF Clock'EVENT AND Clock = '1' THEN
```

```
            Q <= D;
```

```
        END IF;
```

```
    END PROCESS;
```

```
END Behavior;
```


Flip-Flop D com Reset Síncrono

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY flipflop IS
```

```
    PORT (D, Resetn, Clock : IN    STD_LOGIC;
```

```
          Q                 : OUT  STD_LOGIC);
```

```
END flipflop;
```

```
ARCHITECTURE Behavior OF flipflop IS
```

```
BEGIN
```

```
    PROCESS
```

```
    BEGIN
```

```
        WAIT UNTIL Clock'EVENT AND Clock = '1';
```

```
        IF Resetn = '0' THEN
```

```
            Q <= '0';
```

```
        ELSE
```

```
            Q <= D;
```

```
        END IF;
```

```
    END PROCESS;
```

```
END Behavior;
```

Módulo lpm_shiftreg

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
LIBRARY lpm;
USE lpm.lpm_components.all;

ENTITY shift IS
    PORT ( Clock      : IN      STD_LOGIC;
          Reset       : IN      STD_LOGIC;
          Shiftin, Load : IN      STD_LOGIC;
          R            : IN      STD_LOGIC_VECTOR(3 DOWNTO 0);
          Q            : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) );
END shift;

ARCHITECTURE Structure OF shift IS
BEGIN
    instance: lpm_shiftreg
        GENERIC MAP (LPM_WIDTH => 4, LPM_DIRECTION => "RIGHT")
        PORT MAP (data => R, clock => Clock, aclr => Reset,
                 load => Load, shiftin => Shiftin, q => Q );
END Structure;
```

Registrador de 8 bits com Clear Assíncrono

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY reg8 IS
    PORT ( D           : IN    STD_LOGIC_VECTOR(7 DOWNTO 0);
          Resetn, Clock : IN    STD_LOGIC;
          Q           : OUT   STD_LOGIC_VECTOR(7 DOWNTO 0) );
END reg8;

ARCHITECTURE Behavior OF reg8 IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= "00000000";
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D;
        END IF;
    END PROCESS;
END Behavior;
```

Registrador de N bits com Clear Assíncrono

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY regn IS
    GENERIC ( N : INTEGER := 16 );
    PORT (D           : IN  STD_LOGIC_VECTOR(N-1 DOWNT0 0);
          Resetn, Clock : IN  STD_LOGIC;
          Q           : OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0) );
END regn;

ARCHITECTURE Behavior OF regn IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= (OTHERS => '0');
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D;
        END IF;
    END PROCESS;
END Behavior;
```

Flip-flop D com um mux 2:1 na entrada D

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY muxdff IS
    PORT ( D0, D1, Sel, Clock : IN STD_LOGIC;
          Q                   : OUT  STD_LOGIC );
END muxdff;

ARCHITECTURE Behavior OF muxdff IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1';
        IF Sel = '0' THEN
            Q <= D0;
        ELSE
            Q <= D1;
        END IF;
    END PROCESS;
END Behavior;
```

Shift Register

Usando muxdff como Componente

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY shift4 IS
    PORT ( R          : IN          STD_LOGIC_VECTOR(3 DOWNTO 0);
          L, w, Clock : IN          STD_LOGIC;
          Q          : BUFFER      STD_LOGIC_VECTOR(3 DOWNTO 0));
END shift4;

ARCHITECTURE Structure OF shift4 IS
    COMPONENT muxdff
        PORT ( D0, D1, Sel, Clock : IN    STD_LOGIC;
              Q                : OUT    STD_LOGIC );
    END COMPONENT;
BEGIN
    Stage3: muxdff PORT MAP ( w, R(3), L, Clock, Q(3) );
    Stage2: muxdff PORT MAP ( Q(3), R(2), L, Clock, Q(2) );
    Stage1: muxdff PORT MAP ( Q(2), R(1), L, Clock, Q(1) );
    Stage0: muxdff PORT MAP ( Q(1), R(0), L, Clock, Q(0) );
END Structure;
```

Shift Register

Código Alternativo

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY shift4 IS
    PORT ( R      : IN      STD_LOGIC_VECTOR(3 DOWNT0 0);
          Clock  : IN      STD_LOGIC;
          L, w    : IN      STD_LOGIC;
          Q      : BUFFER  STD_LOGIC_VECTOR(3 DOWNT0 0) );
END shift4;
```

```
ARCHITECTURE Behavior OF shift4 IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1';
        IF L = '1' THEN
            Q <= R;
        ELSE
            Q(0) <= Q(1);
            Q(1) <= Q(2);
            Q(2) <= Q(3);
            Q(3) <= w;
        END IF;
    END PROCESS;
END Behavior;
```

Registrador N bits com Saída Tri-state


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY trin IS
    GENERIC ( N : INTEGER := 8 );
    PORT ( X   : IN   STD_LOGIC_VECTOR(N-1 DOWNTO 0);
          E   : IN   STD_LOGIC;
          F   : OUT  STD_LOGIC_VECTOR(N-1 DOWNTO 0) );
END trin;

ARCHITECTURE Behavior OF trin IS
BEGIN
    F <= (OTHERS => 'Z') WHEN E = '0' ELSE X;
END Behavior;
```



Projeto de Máquina de Estados

Exemplo:

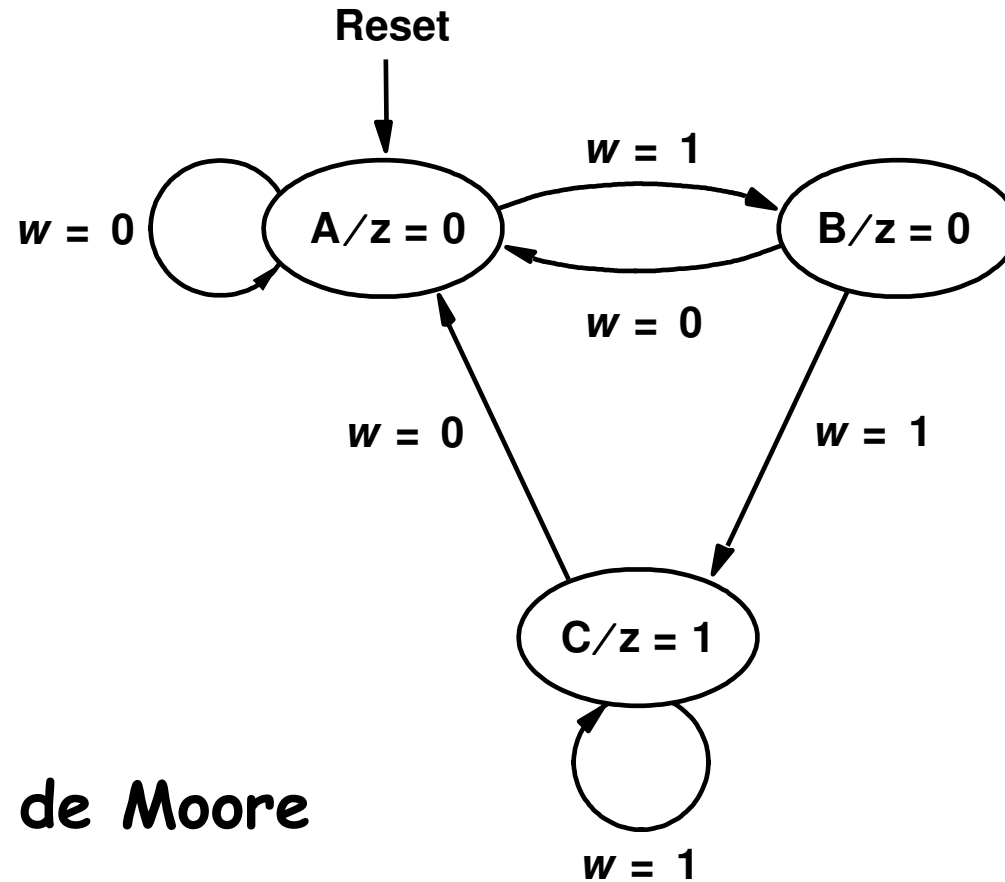 

Máquina de Moore

Projeto de Máquina de Estados Exemplo:



Máquina de Mealy

FSM de Moore

```
USE ieee.std_logic_1164.all;
```

```
ENTITY simple IS
```

```
    PORT (Clock, Resetn, w : IN    STD_LOGIC;  
          z                : OUT   STD_LOGIC );
```

```
END simple;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    TYPE State_type IS (A, B, C); -- Tipo Enumerado para  
                                   -- definir os Estados
```

```
    SIGNAL y : State_type;
```

```
BEGIN
```

```
    PROCESS ( Resetn, Clock )
```

```
    BEGIN
```

```
        IF Resetn = '0' THEN -- A é o estado inicial
```

```
            y <= A;
```


```
        ELSIF (Clock'EVENT AND Clock = '1') THEN
```

```
con't ...
```


FSM de Moore

```
CASE y IS
  WHEN A =>
    IF w = '0'
      THEN y <= A;
      ELSE y <= B;
    END IF;
  WHEN B =>
    IF w = '0'
      THEN y <= A;
      ELSE y <= C;
    END IF;
  WHEN C =>
    IF w = '0'
      THEN y <= A;
      ELSE y <= C;
    END IF;
  END CASE;
END IF;
END PROCESS;
z <= '1' WHEN y = C ELSE '0';
END Behavior;
```


FSM de Moore - Simulação

 

FSM de Moore - Simulação

 

FSM de Moore Simulação

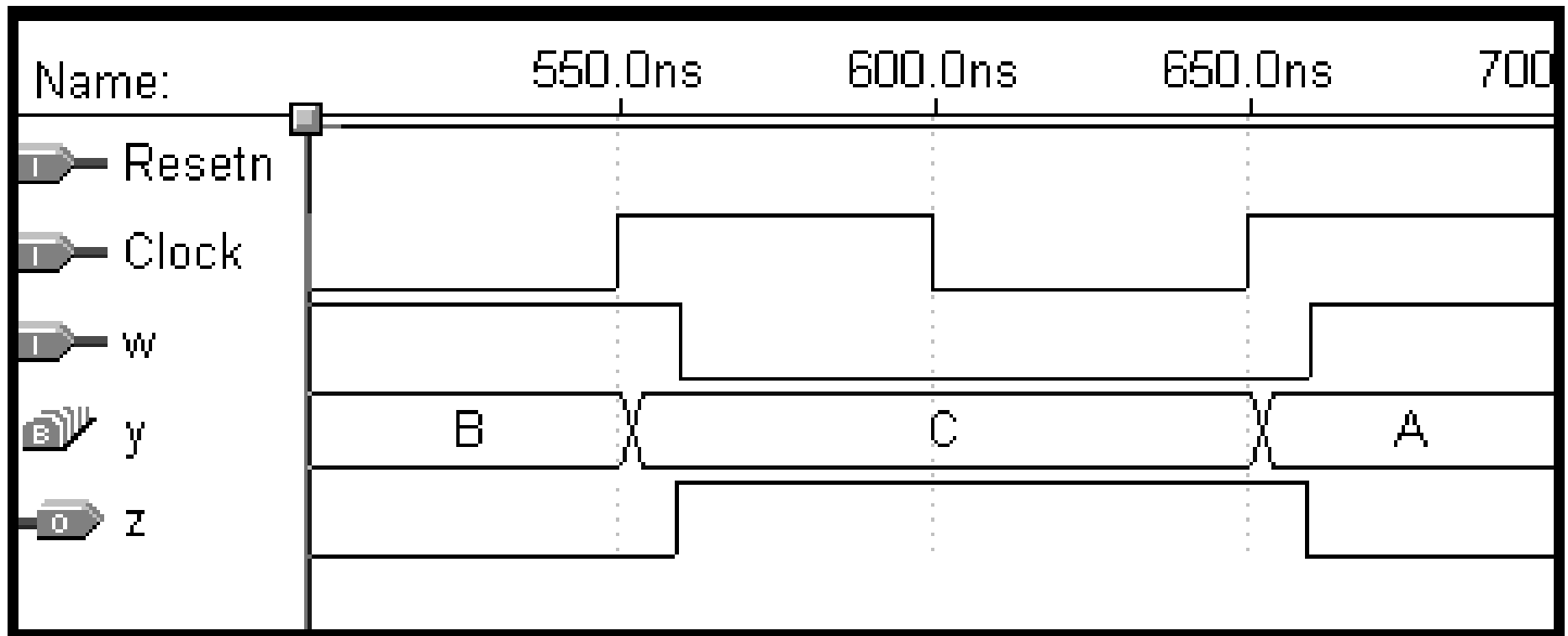

FSM de Moore

Codificação Alternativa (2 processos)

```
USE ieee.std_logic_1164.all;
```

```
ENTITY simple IS
```

```
    PORT (Clock, Resetn, w : IN    STD_LOGIC;  
          z                : OUT  STD_LOGIC );
```

```
END simple;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    TYPE State_type IS (A, B, C);
```

```
SIGNAL y_present, y_next : State_type;
```


FSM de Moore

Codificação Alternativa (2 processos)

```
BEGIN
  PROCESS ( w, y_present )
  BEGIN
    CASE y_present IS
      WHEN A =>
        IF w = '0' THEN
          y_next <= A;
        ELSE
          y_next <= B;
        END IF;
      WHEN B =>
        IF w = '0' THEN
          y_next <= A;
        ELSE
          y_next <= C;
        END IF;
    END CASE;
  END PROCESS;
END;
```

FSM de Moore

Codificação Alternativa (2 processos)

```
    WHEN C =>
        IF w = '0' THEN
            y_next <= A;
        ELSE
            y_next <= C;
        END IF;
    END CASE;
END PROCESS;
```

```
PROCESS (Clock, Resetn)
BEGIN
    IF Resetn = '0' THEN
        y_present <= A;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next;
    END IF;
END PROCESS;
```

```
z <= '1' WHEN y_present = C ELSE '0';
END Behavior;
```

FSM

O Usuário Especificando a Atribuição de Estados

```
ARCHITECTURE Behavior OF simple IS
```

```
TYPE State_TYPE IS (A, B, C);
```

```
ATTRIBUTE ENUM_ENCODING : STRING;
```

```
ATTRIBUTE ENUM_ENCODING OF State_type : TYPE IS "00 01 11";
```

```
SIGNAL y_present, y_next : State_type;
```

```
BEGIN
```

```
con't ...
```

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
ENTITY simple IS
```

```
    PORT ( Clock, Resetn, w : IN    STD_LOGIC;  
          z                  : OUT  STD_LOGIC );
```

```
END simple;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    SIGNAL y_present, y_next : STD_LOGIC_VECTOR(1 DOWNTO 0);  
    CONSTANT A  : STD_LOGIC_VECTOR(1 DOWNTO 0) := "00";  
    CONSTANT B  : STD_LOGIC_VECTOR(1 DOWNTO 0) := "01";  
    CONSTANT C  : STD_LOGIC_VECTOR(1 DOWNTO 0) := "11";
```

```
BEGIN
```

```
    PROCESS ( w, y_present )  
    BEGIN
```

```
        CASE y_present IS
```

```
            WHEN A =>
```

```
                IF w = '0' THEN y_next <= A;
```

```
                ELSE y_next <= B;
```

```
                END IF;
```

```
... con't
```

```

        WHEN B =>
            IF w = '0' THEN y_next <= A;
            ELSE y_next <= C;
            END IF;
        WHEN C =>
            IF w = '0' THEN y_next <= A;
            ELSE y_next <= C;
            END IF;
        WHEN OTHERS =>
            y_next <= A;
    END CASE;
END PROCESS;

PROCESS ( Clock, Resetn )
BEGIN
    IF Resetn = '0' THEN
        y_present <= A;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next;
    END IF;
END PROCESS;
z <= '1' WHEN y_present = C ELSE '0';
END Behavior;

```

FSM de Mealy

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
ENTITY mealy IS  
    PORT (Clock, Resetn, w : IN  STD_LOGIC;  
          z                : OUT STD_LOGIC );  
END mealy;
```

```
ARCHITECTURE Behavior OF mealy IS  
    TYPE State_type IS (A, B);  
    SIGNAL y : State_type;
```

```
BEGIN
```

```
    PROCESS ( Resetn, Clock )  
    BEGIN
```

```
        IF Resetn = '0' THEN  
            y <= A;
```

```
        ELSIF (Clock'EVENT AND Clock = '1') THEN  
            CASE y IS
```

```
                WHEN A =>
```

```
                    IF w = '0' THEN y <= A;  
                    ELSE y <= B;  
                    END IF;
```

```
... con't
```

FSM de Mealy

```
                WHEN B =>
                    IF w = '0' THEN y <= A;
                    ELSE y <= B;
                    END IF;
            END CASE;
    END IF;
END PROCESS;

PROCESS ( y, w )
BEGIN
    CASE y IS
        WHEN A =>
            z <= '0';
        WHEN B =>
            z <= w;
    END CASE;
END PROCESS;
END Behavior;
```