

Sequential Logic & SystemVerilog

Rodolfo Azevedo

Institute of Computing, University of Campinas (UNICAMP), Brazil

rodolfo.azevedo@unicamp.br

<http://www.ic.unicamp.br/~rodolfo/mo801>

Goal of this class

Module 1, Class 3: latches, flip-flops, registers, counters — and `always_ff`.

Combinational circuits compute functions of *current* inputs. Sequential circuits also remember the *past*. This class introduces the element that makes memory possible: the flip-flop — and the SystemVerilog construct `always_ff` that describes it.

At the end of this class, you should be able to:

- Explain the D flip-flop's setup time, hold time, and propagation delay, and why violating them causes metastability.
- Write synchronous sequential circuits using `always_ff` with non-blocking assignments.
- Implement registers, counters, and the two-process pattern in SystemVerilog.
- Apply a two-FF synchronizer to safely bring asynchronous inputs into a synchronous design.
- Analyze clock timing constraints ($t_{pcq} + t_{comb} + t_{su}$) and interpret nextpnr timing reports.


Why we need memory: the latch

Consider a traffic light controller. The output (which light is on) depends not only on a push-button but also on *which state the light was in before*. That is sequential behaviour — the circuit needs to remember something.

The simplest memory element is the **SR latch** (Set-Reset), built from two cross-coupled NAND gates:

S	R	Q (next)
0	0	Q (hold)
0	1	0 (reset)
1	0	1 (set)
1	1	undefined

 The undefined state and level-sensitive (not edge-triggered) behaviour make raw latches difficult to use reliably in synchronous designs. **In practice, we use flip-flops.**




The D flip-flop: edge-triggered memory

A **D flip-flop** (DFF) samples its input D at the **rising edge** of the clock and holds it until the next rising edge:

- **Setup time** (t_{su}): D must be stable *before* the rising edge.
- **Hold time** (t_h): D must stay stable *after* the rising edge.
- **Propagation delay** (t_{pcq}): time from clock edge to valid Q .

Violating setup or hold time causes **metastability** — the flip-flop output is unpredictable. This is why you cannot connect two independent clock domains directly without a synchronizer.

 The DFF is the fundamental building block of all synchronous digital design. Every register, every FSM state, every pipeline stage is a collection of DFFs.



The two-flip-flop synchronizer

Any signal that crosses a clock domain boundary — or comes from outside the chip entirely (button press, UART RX) — can arrive at any phase relative to the destination clock. If it violates the DFF's setup or hold time, the output may **never settle to a valid 0 or 1**: this is called **metastability**.

Solution: cascade two DFFs clocked by the destination domain.

```
module sync2ff #(parameter WIDTH = 1) (  
    input  logic      clk,  
    input  logic [WIDTH-1:0] async_in,  
    output logic [WIDTH-1:0] sync_out  
);  
    logic [WIDTH-1:0] meta;  
    always_ff @(posedge clk) begin  
        meta      <= async_in;    // stage 1: may be metastable  
        sync_out <= meta;        // stage 2: stable with high probability  
    end  
endmodule
```

- The first FF can go metastable, but has a full clock period to settle before stage 2 samples it.
- **Rule:** every asynchronous input — button, UART RX line, any cross-domain signal — must pass through a synchronizer before any logic uses it.
- Two FFs suffice for most FPGA frequencies (≤ 100 MHz). Very high-speed designs use three.

Level detection vs. edge detection

Level detection: logic acts every cycle that a signal holds a value.

```
if (btn_sync == 1) ... // fires every clock while button is held – usually wrong
```

Edge detection: logic acts exactly once, on the transition. Implemented by comparing the current value to a one-cycle-delayed copy:

```
logic btn_prev, btn_rising;
always_ff @(posedge clk)
    btn_prev <= btn_sync;

assign btn_rising = btn_sync & ~btn_prev; // one-cycle pulse on rising edge
```

Why it matters for **UART RX**:

- The receiver must detect the **falling edge of the START bit**, then count half a bit-period to reach the centre of bit 0.
- Level detection would re-trigger the receiver on every cycle the line is low.
- Edge detection fires once; a counter then times out to the sample point.

Common bug: using level detection for a button → an action (e.g., counter increment) repeats millions of times per second while the button is held.

always_ff — describing flip-flops in SystemVerilog

```
module dff (  
    input logic clk, rst, d,  
    output logic q  
);  
    always_ff @(posedge clk) begin  
        if (rst)  
            q <= 1'b0;    // synchronous reset  
        else  
            q <= d;  
    end  
endmodule
```

Key rules for `always_ff`:

- Use **non-blocking assignment** `<=` — never `=` inside `always_ff`.
- The sensitivity list must be `@(posedge clk)` (or `@(negedge clk)` for falling-edge). Tools reject other patterns.
- The synthesis tool maps this directly to a flip-flop primitive in the target technology.

Synchronous vs. asynchronous reset

Both styles are common; your project's choice must be consistent throughout:

```
// Synchronous reset – reset only takes effect on the clock edge
always_ff @(posedge clk) begin
    if (rst) q <= '0;
    else     q <= d;
end

// Asynchronous reset – reset takes effect immediately, regardless of clock
always_ff @(posedge clk or posedge rst) begin
    if (rst) q <= '0;
    else     q <= d;
end
```

- **Synchronous reset:** simpler timing analysis, easier to synthesize; requires a clock edge to release reset. Preferred for most student designs.
- **Asynchronous reset:** can reset even with no clock running; adds a separate path through the flip-flop's `rst` pin.
- `'0` is the **aggregate zero literal** — fills the entire left-hand side with zeros, regardless of width. Equivalent to `4'b0000` for a 4-bit signal but works for any width.

Non-blocking assignment — why it matters

Wrong: produces a shift register in simulation, but models wrong hardware intent with blocking '='

```
always_ff @(posedge clk) begin
    b = a;    // b gets new a
    c = b;    // c gets new b — which is already updated!
end
```

Correct: both sample simultaneously at the clock edge

```
always_ff @(posedge clk) begin
    b <= a;
    c <= b;    // c gets old b (the value b held before this edge)
end
```

The rule is simple and absolute

- **<=** (non-blocking) inside **always_ff** — models registers: all right-hand sides are evaluated first using old values, then all assignments happen simultaneously.
- **=** (blocking) inside **always_comb** — models wires: evaluation proceeds top-to-bottom like sequential software.

Mixing the two inside one block is a synthesis error.

Registers: N flip-flops sharing a clock

An N -bit register is N DFFs with a shared clock and reset:

```
module register #(parameter WIDTH = 32) (  
    input logic      clk, rst,  
    input logic [WIDTH-1:0] d,  
    output logic [WIDTH-1:0] q  
);  
    always_ff @(posedge clk) begin  
        if (rst) q <= '0;  
        else     q <= d;  
    end  
endmodule
```

With an enable signal (load only when `en` is high):

```
always_ff @(posedge clk) begin  
    if (rst)      q <= '0;  
    else if (en)  q <= d;  
    // else: q holds its value  
end
```

This pattern — register with synchronous reset and enable — is the template for every register in the RV32I datapath: `PC`, `IR`, `MDR`, `ALUOUT`, and the 32 general-purpose registers.

Shift register

A **serial-in, serial-out (SISO)** shift register delays a 1-bit signal by N clock cycles:

```
module shift_reg #(parameter DEPTH = 8) (  
    input logic clk, rst,  
    input logic d,  
    output logic q  
);  
    logic [DEPTH-1:0] sr;  
    always_ff @(posedge clk) begin  
        if (rst) sr <= '0;  
        else     sr <= {sr[DEPTH-2:0], d};    // shift left; new bit enters at LSB  
    end  
    assign q = sr[DEPTH-1];                    // output: the oldest bit  
endmodule
```

- `{sr[DEPTH-2:0], d}` is concatenation: drop the MSB (which exits as `q`) and append the new input at the LSB.
- After N cycles of stable input `d`, `q` equals `d`. This is a N -cycle pipeline delay.

Applications in this course

- **UART TX:** the transmitter loads an 8-bit byte into a shift register and shifts one bit per baud period onto the TX line (M03A03).
- **SPI:** master and slave exchange bits simultaneously through a shared shift register pair.
- **Depth-1:** a single DFF — the atomic pipeline stage. Every pipeline register in Project 3's accelerator is a shift register of depth 1.

Counters

A synchronous counter increments its value every clock cycle:

```
module counter #(parameter WIDTH = 25) (  
    input logic      clk, rst,  
    output logic [WIDTH-1:0] count  
);  
    always_ff @(posedge clk) begin  
        if (rst) count <= '0;  
        else     count <= count + 1'b1;  
    end  
endmodule
```

- A 25-bit counter on a 27 MHz clock overflows every $2^{25}/27 \text{ MHz} \approx 1.24$ seconds — slow enough to see on an LED.
- The most significant bit `count[24]` toggles at half that rate (once every ~0.62 s), giving a visible blink.
- Asynchronous counters (each FF clocked by the previous FF's output) exist but are harder to time and not used in synchronous designs.

In-class exercise — sequential circuits

Extend the basic counter with `load` and `en` control inputs:

rst	load	en	Behaviour
1	x	x	Synchronous reset → 0
0	1	x	Load the value on <code>d</code>

```
module counter_le #(parameter WIDTH = 4) (  
    input logic      clk, rst, load, en,  
    input logic [WIDTH-1:0] d,  
    output logic [WIDTH-1:0] count  
);  
    always_ff @(posedge clk) begin  
        // your code here – three branches in priority order  
    end  
endmodule
```

Trace on paper (start `count = 4'h3`): apply `load=1, d=4'hA`; then `en=1` for 3 cycles; then `en=0` for 1 cycle. Write `count` after each clock edge.

Expected sequence: `3 → A → B → C → D → D`. Any difference? Check the priority of your `if / else if` branches — the order matters.

The two-process pattern

Separating state storage from next-state logic keeps code readable and synthesizable:

```
module up_counter #(parameter WIDTH = 4) (  
    input logic      clk, rst, en,  
    output logic [WIDTH-1:0] count  
);  
    logic [WIDTH-1:0] count_next;  
  
    // Process 1: register (state storage)  
    always_ff @(posedge clk) begin  
        if (rst) count <= '0;  
        else    count <= count_next;  
    end  
  
    // Process 2: next-state logic (combinational)  
    always_comb begin  
        count_next = count;          // default: hold  
        if (en) count_next = count + 1'b1;  
    end  
endmodule
```

This two-process pattern is the standard template for FSMs (next class) and datapath components. The `always_ff` block is always trivial; all the interesting logic lives in `always_comb`.

Timing: clock period and maximum frequency

The clock period must be long enough for the longest combinational path between two registers:

$$T_{clk} \geq t_{pcq} + t_{comb} + t_{su}$$

where

- t_{pcq} is the flip-flop propagation delay
- t_{comb} is the combinational delay through logic
- t_{su} is the setup time of the destination flip-flop.

After place-and-route, nextpnr reports the **worst negative slack (WNS)**:

- $WNS \geq 0 \rightarrow$ timing met at the requested frequency
- $WNS < 0 \rightarrow$ timing violated; reduce frequency or shorten the critical path

The Tang Nano 9K runs at 27 MHz. A minimal RV32I core easily meets 27 MHz. But if you add a deep combinational path (e.g., a multi-cycle multiplier in the ALU), you may need to pipeline it.

Board exercise — LED blink counter

```
module blink (  
    input logic      clk,      // 27 MHz oscillator  
    input logic      rst_n,    // active-low reset (Tang Nano button)  
    output logic [5:0] led      // active-low LEDs  
);  
    logic [24:0] count;  
  
    always_ff @(posedge clk) begin  
        if (~rst_n) count <= '0;  
        else        count <= count + 1'b1;  
    end  
  
    // MSB toggles at ~0.8 Hz; each lower bit is twice as fast  
    assign led[0] = ~count[24];  
    assign led[1] = ~count[23];  
    assign led[2] = ~count[22];  
    assign led[3] = ~count[21];  
    assign led[4] = ~count[20];  
    assign led[5] = ~count[19];  
endmodule
```

Synthesize and load. You should see LEDs blinking at different rates — a direct visualization of binary counting.

Signal naming convention

Consistent names make code readable and catch bugs at review time. The conventions below are used throughout this course and match industry practice.

Signal	Convention	Example	Notes
Clock	<code>clk</code>	<code>clk</code> , <code>clk_fast</code>	One clock per domain; prefix if multiple
Reset, active-high	<code>rst</code>	<code>rst</code>	Asserted when 1; released on clock edge (sync)
Reset, active-low	<code>rst_n</code>	<code>rst_n</code>	<code>_n</code> suffix = active-low; 0 means reset
Enable	<code>en</code> or <code>*_en</code>	<code>uart_en</code> , <code>cnt_en</code>	Allows operation when 1
Write enable	<code>we</code>	<code>regfile_we</code>	Enables a write on the next rising edge
Chip select	<code>cs_n</code>	<code>sram_cs_n</code>	Active-low select; common in memory interfaces
Data valid	<code>valid</code>	<code>rx_valid</code>	Producer asserts: "this data is good right now"
Ready	<code>ready</code>	<code>tx_ready</code>	Consumer asserts: "I can accept data right now"
Load / latch	<code>load</code>	<code>ir_load</code>	Capture input into a register this cycle
Done / done flag	<code>done</code>	<code>mult_done</code>	One-cycle pulse when an operation completes
Next-state copy	<code>*_next</code>	<code>state_next</code> , <code>pc_next</code>	Combinational; wired to the <code><=</code> in <code>always_ff</code>

Signal naming convention (continued)

Active-low signals

- Carry the `_n` suffix and are driven 0 to assert
- The Tang Nano 9K buttons and LEDs are active-low (`btn[0]` pressed $\rightarrow$ 0; `led[0]` on $\rightarrow$ 0)

Edge convention in names

- `posedge clk` = rising-edge clocked (default)
- `negedge clk` = falling-edge
- Write `clk_n` only when referring to the inverted clock line itself, not to falling-edge sensitivity

Next class

FSMs in SystemVerilog: Moore and Mealy machines, state encoding with `typedef enum`, and `typedef struct packed` for grouping control signals — exactly the patterns you will use in Project 1's control FSM.