

The Multicycle Datapath

Rodolfo Azevedo

Institute of Computing, University of Campinas (UNICAMP), Brazil

rodolfo.azevedo@unicamp.br

<http://www.ic.unicamp.br/~rodolfo/mo801>

Goal of this class

Module 2, Class 2: building a RV32I datapath one cycle at a time.

Last class was "what an instruction means." Today is "what hardware do we need to execute it, and why does it take more than one cycle." By the end, you'll have the component-level picture your Project 1 datapath needs to instantiate and wire together.

At the end of this class, you should be able to:

- Break any RV32I instruction into its fetch, decode, execute, memory, and writeback steps.
- Identify the hardware components of the multicycle datapath and the control signals that steer them.
- Draw the datapath diagram and trace the data flow for R-type, I-type, load, store, and branch instructions.
- Map datapath components (ALU, register file, memory, PC) to the SystemVerilog modules built in M01.

Why multicycle?


- A **single-cycle** datapath executes every instruction in one clock cycle - simple to reason about, but the cycle time must be long enough for the *slowest* instruction (typically a memory access), wasting time on every other instruction.
- A **multicycle** datapath breaks execution into several shorter steps (cycles), each doing one "unit" of work (a register read, an ALU operation, a memory access, ...). Different instructions take different numbers of cycles - simple instructions finish sooner.
- This matches our SystemVerilog toolkit directly: each cycle is one step of an `always_ff`-driven **control FSM** (M01A02's two-process pattern), and the datapath components are the combinational logic and registers it controls.

The five canonical steps

Most RV32I instructions can be executed as a subset of these steps:

1. **Fetch**: read the instruction word from instruction memory at `PC` ; compute `PC + 4` .
 2. **Decode**: split the instruction into fields (M02A01's formats); read `rs1` / `rs2` from the register file; reassemble any immediate.
 3. **Execute**: the ALU computes a result - `rs1 + rs2` , `rs1 + imm` , a branch comparison, an address, ...
 4. **Memory**: for loads/stores, access data memory at the address computed in step 3.
 5. **Write-back**: write a result into `rd` (the ALU result, loaded data, or `PC+4` for `JAL` / `JALR`).
- `ADD` needs steps 1-3 and 5 (no memory). `LW` needs all five. `BEQ` needs 1-3 (compare, then conditionally update `PC` - no register write-back). Different instructions = different *paths* through the same steps.

The multicycle datapath — state elements

 


Multicycle datapath -- state-holding elements (registers), in dataflow order. ALU and the two memories are combinational/read-only from this view.

The datapath components

```
flowchart LR
    PC[PC register] --> IMEM[Instruction memory]
    IMEM --> IR[Instruction register]
    IR --> RF[Register file]
    RF --> ALU
    IR --> |immediate| ALU
    ALU --> ALUOUT[ALU result register]
    ALUOUT --> DMEM[Data memory]
    DMEM --> MDR[Memory data register]
    ALUOUT --> RF
    MDR --> RF
    ALUOUT --> PC
```

- **PC, IR, ALUOUT, MDR:** the "extra" registers a multicycle design needs beyond the architectural register file - they hold intermediate values *between* cycles, so each cycle's combinational logic only needs to look at the *previous* cycle's results.
- **Register file:** from M02A01 - 32 x 32-bit, `x0` hardwired to 0. Typically one write port, one or two read ports.
- **ALU:** the same kind of module as M01A01's `alu1`, but wider (32-bit) and with more operations (add, subtract, compare, shift, AND/OR/XOR - enough to cover all RV32I ALU ops).
- **Instruction memory / data memory:** for Project 1, can start as simple synchronous-read `logic` arrays (BRAM-friendly) - see M01A04 for resource budget.

Complete multicycle datapath

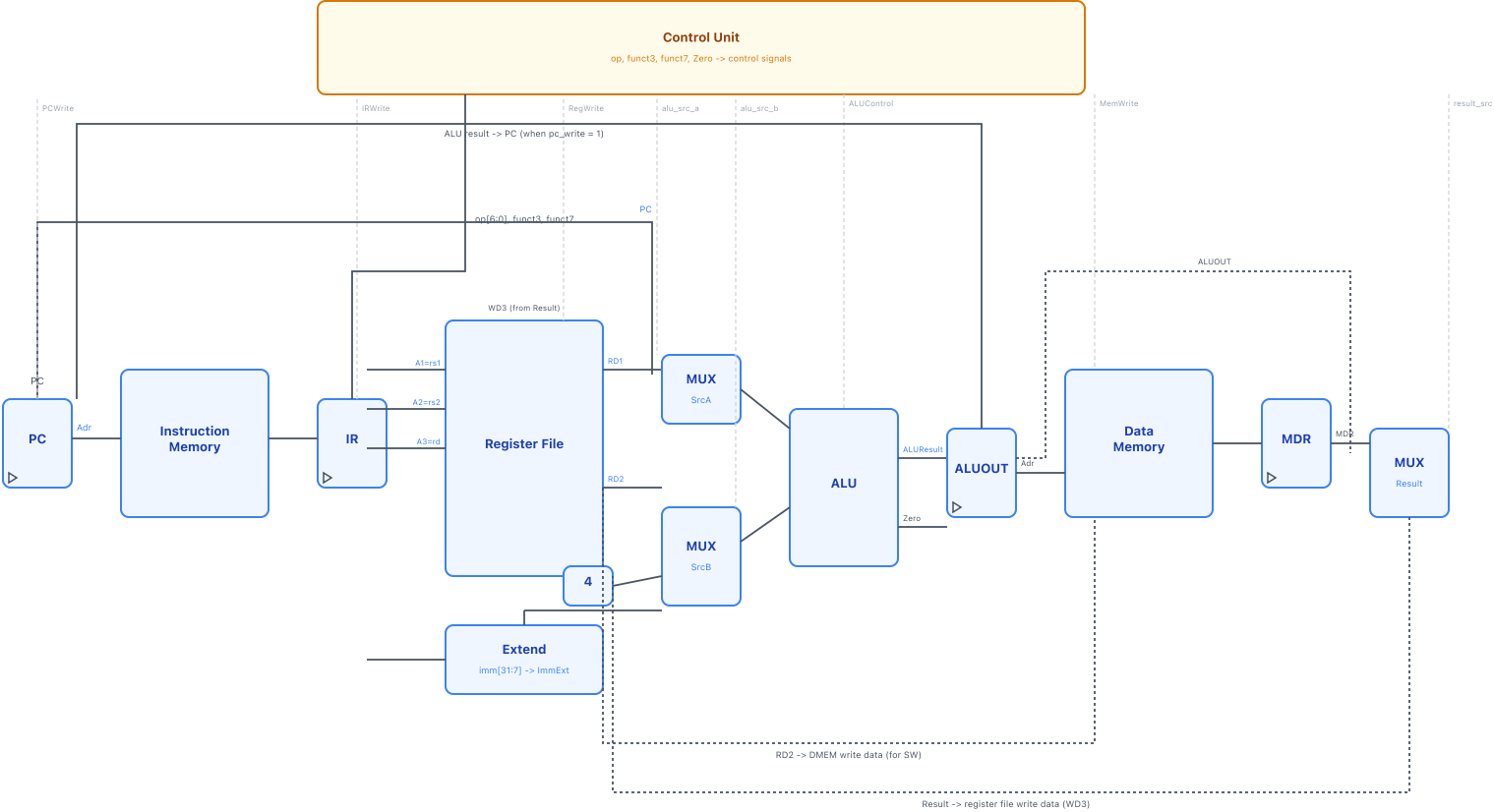

Complete multicycle datapath (Harvard IMEM/DMEM split)

Why the extra registers?

Consider `LW rd, imm(rs1) : address = rs1 + imm` (an ALU operation), then `mem[address]` (a memory operation), then `rd = mem[address]` (a register write) - **three** operations that each take one cycle.

```
// Cycle 3 (Execute): compute the address
always_ff @(posedge clk)
    if (state == EXECUTE)
        alu_out <= rs1_val + imm;    // ALUOUT register captures the address

// Cycle 4 (Memory): use the captured address
always_ff @(posedge clk)
    if (state == MEMORY)
        mdr <= data_mem[alu_out];    // MDR register captures the loaded word
```

- Without `alu_out` and `mdr`, the address computed in cycle 3 would be lost by cycle 4 - it exists only as a combinational signal during cycle 3.
- This is the **register + combinational logic** pattern from M01A02, applied at the datapath level: every value that must survive to a later cycle needs its own register.

Control signals: the datapath's "knobs"

The datapath components don't decide anything by themselves - they're driven by **control signals** that the FSM (M02A03) sets each cycle:

Signal	Controls
<code>pc_write</code>	Does <code>PC</code> update this cycle?
<code>ir_write</code>	Does the instruction register latch the fetched word?
<code>alu_op</code>	Which operation does the ALU perform?
<code>alu_src_a</code> , <code>alu_src_b</code>	What feeds the ALU's inputs (register, immediate, <code>PC</code> , constant <code>4</code>)?
<code>mem_read</code> , <code>mem_write</code>	Access data memory this cycle?
<code>reg_write</code> , <code>reg_dst</code> , <code>result_src</code>	Write the register file this cycle, and from where?

- Each signal is one bit (or a small `enum`) computed by `always_comb` in the control FSM, based on the current `state` and the decoded `opcode` / `funct3` / `funct7` .
- This is the same `enum` + `always_comb` + `case` pattern from M01A02's FSM example - just with many more outputs per state.

Control signals per state — reference table

The FSM sets these signals on every clock cycle. A `—` means "don't care / unchanged":

State	pc_write	ir_write	alu_src_a	alu_src_b	alu_op	mem_read	mem_write	reg_write	result_src
FETCH	1	1	PC	4	ADD	IMEM	0	0	—
DECODE	0	0	—	—	—	0	0	0	—
EXEC_R	0	0	RS1	RS2	funct7/3	0	0	0	—
EXEC_I	0	0	RS1	IMM	funct3	0	0	0	—
EXEC_BRANCH	cond	0	RS1	RS2	SUB	0	0	0	—
MEM_ADDR	0	0	RS1	IMM	ADD	0	0	0	—
MEM_READ	0	0	—	—	—	DMEM	0	0	—
MEM_WRITE	0	0	—	—	—	0	DMEM	0	—

- `pc_write = cond` in `EXEC_BRANCH` means "write PC only if the branch condition is true."
- This table is the **specification for your Project 1 control FSM** — each row becomes one `case` arm in `always_comb`.
- Signals left as `—` can keep their default value (set at the top of `always_comb`) — same discipline as the accidental-latch fix from M01A02.

Putting it together: one ALU input mux

```
typedef enum logic [1:0] { ALU_SRC_A_RS1, ALU_SRC_A_PC } alu_src_a_t;
typedef enum logic [1:0] { ALU_SRC_B_RS2, ALU_SRC_B_IMM, ALU_SRC_B_4 } alu_src_b_t;

logic [31:0] alu_a, alu_b;

always_comb begin
    case (alu_src_a)
        ALU_SRC_A_RS1: alu_a = rs1_val;
        ALU_SRC_A_PC:  alu_a = pc;
        default:       alu_a = rs1_val;
    endcase
    case (alu_src_b)
        ALU_SRC_B_RS2: alu_b = rs2_val;
        ALU_SRC_B_IMM: alu_b = imm;
        ALU_SRC_B_4:   alu_b = 32'd4;
        default:       alu_b = rs2_val;
    endcase
end
```

- `alu_src_a` / `alu_src_b` are control signals set by the FSM. The same physical ALU computes `rs1 + rs2` (for `ADD`), `rs1 + imm` (for `LW`'s address), `PC + imm` (for `BEQ`'s target), and `PC + 4` (for the next-PC default) - just by changing what feeds it.
- **This is the heart of "multicycle"**: one ALU, reused across cycles for different purposes, instead of separate adders for each.

Instruction trace: `ADD x3, x1, x2`

Cycle-by-cycle walk-through (4 cycles total):

Cycle	State	Key datapath action	What updates
1	FETCH	<code>IR ← mem[PC]</code> ; <code>PC ← PC+4</code> via ALU	IR, PC
2	DECODE	read <code>rs1=x1</code> , <code>rs2=x2</code> ; decode R-type; <code>state_next = EXEC_R</code>	(combinational)
3	EXEC_R	ALU computes <code>x1 + x2</code> ; result → ALUOUT	ALUOUT
4	WRITEBACK_ALU	<code>x3 ← ALUOUT</code> ; <code>state_next = FETCH</code>	register file

Control signals in cycle 3: `alu_src_a=RS1` , `alu_src_b=RS2` , `alu_op=ADD` , `reg_write=0` (not yet).

Control signals in cycle 4: `reg_write=1` , `result_src=ALUOUT` , `reg_dst=rd` .

Every R-type and I-type ALU instruction follows this exact 4-cycle template. The FSM reuses the same states — only the `alu_op` and the source of `alu_src_b` differ.

Instruction trace: LW x3, 8(x1)

The most complex instruction — 5 cycles:

Cycle	State	Key datapath action	What updates
1	FETCH	$IR \leftarrow \text{mem}[PC]$; $PC \leftarrow PC+4$	IR, PC
2	DECODE	read $rs1=x1$; sign-extend $\text{imm}=8$; $\text{state_next} = \text{MEM_ADDR}$	(combinational)
3	MEM_ADDR	ALU: $x1 + 8 \rightarrow \text{ALUOUT}$ (the load address)	ALUOUT
4	MEM_READ	$\text{MDR} \leftarrow \text{data_mem}[\text{ALUOUT}]$	MDR
5	WRITEBACK_MEM	$x3 \leftarrow \text{MDR}$; $\text{state_next} = \text{FETCH}$	register file

- **MEM_ADDR** is **shared with SW** — both compute $rs1 + \text{imm}$; the next state distinguishes load from store.
- **MDR** (Memory Data Register) exists precisely so the loaded value survives from cycle 4 to cycle 5.
- Without **MDR** , **data_mem** output would need to remain stable for two cycles — which is harder to guarantee and wastes a memory port.

In-class exercise — datapath trace

Exercise (10 min): trace `SW x2, 12(x1)` (store `x2` to address `x1 + 12`) through the datapath.

Fill in the table:

Cycle	State	Key datapath action	What updates
1			
2			
3			
4			

Questions:

1. Which control signals differ from `LW` in cycles 3–4?
2. Does `reg_write` ever go high during `SW`? Why or why not?
3. Why does `SW` use only 4 cycles while `LW` uses 5?

Expected: `FETCH` → `DECODE` → `MEM_ADDR` (`x1+12` → `ALUOUT`) → `MEM_WRITE` (`data_mem[ALUOUT] ← x2`).
`reg_write` is never 1 — stores write memory, not registers. No `WRITEBACK` state needed.

Next class

Designing the Control FSM: the `enum` of states, the `case`-based control logic that drives every signal from the table above, and a cycle-by-cycle trace of `ADDI`, `LW`, and `BEQ` through the datapath.